

Lab Preliminary Report

Course: Cs 223 Digital
Design

Section: 2

Lab Number: 3

Name: Eralp Yiğit Boz

ID: 22403188

Date: 13.04.2026

Queue Depth Justification: A 3-bit queue counter was chosen, allowing a maximum queue depth of 7 (plus 1 currently processing, totaling 8 requests per machine). Practically, having more than 7 people waiting for a single machine is highly unlikely. Technically, using a 3-bit counter instead of a larger one minimizes the use of FPGA resources (Flip-Flops and LUTs), resulting in a more hardware-efficient design.

Question 1) Indicate which type of FSM (Moore or Mealy) you will implement and justify your choice.

I believe Moore is the most suitable type for this system. I have two reasons for this:

1) Output Stability: In Mealy machines, outputs are directly dependent on instantaneous inputs. This means that if there are glitches in the inputs, this error will be directly reflected in the FSM outputs. In the system we built, the FSM outputs trigger the Timer and Queue in the Datapath. If I had designed it with Mealy, millisecond delays in the buttons could have broken the system. In a Moore Machine, since the outputs are only dependent on registers, small delays will not cause problems.

2) Design Complexity: The lab PDF asks us to shorten the combinational logic part of the system using a decoder. A Moore FSM aligns perfectly with this requirement. Since Moore outputs depend exclusively on the current state, we can connect the state register bits directly to the decoder and use the decoder's output pins as our 'Request' signals to the Datapath without needing any extra logic gates. If a Mealy machine were used, we would have to combine the decoder outputs with the current button inputs using extra AND gates. This would increase the combinational logic and contradict the lab's goal of simplification.

Question 2) Provide the state transition diagram, state encoding, state transition and output tables, next-state and output equations, and the FSM schematic.

2.1) State Encoding

State Name	Q2	Q1	Q0
S0_IDLE	0	0	0
S_REQ_QUICKWASH	0	0	1
S_REQ_HEAVYWASH	0	1	0
S_REQ_DRYER	0	1	1
S_REQ_DELICATEWASH	1	0	0

2.2) State Transition Table

Current State	Pulse_ Q	Pulse_ H	Pulse_D R	Pulse_D W	Next State
S0_IDLE	1	X	X	X	S_REQ_QUICKWASH
S0_IDLE	0	1	X	X	S_REQ_HEAVYWASH
S0_IDLE	0	0	1	X	S_REQ_DRYER
S0_IDLE	0	0	0	1	S_REQ_DELICATEWASH
S0_IDLE	0	0	0	0	S0_IDLE
S_REQ_QUICKWASH	X	X	X	X	S0_IDLE
S_REQ_HEAVYWASH	X	X	X	X	S0_IDLE
S_REQ_DRYER	X	X	X	X	S0_IDLE
S_REQ_DELICATEWASH	X	X	X	X	S0_IDLE

2.3) Output Table

Current State	Req_Q	Req_H	Req_DR	Req_DW
S0_IDLE	0	0	0	0

S_REQ_QUICKWASH	1	0	0	0
S_REQ_HEAVYWASH	0	1	0	0
S_REQ_DRYER	0	0	1	0
S_REQ_DELICATEWASH	0	0	0	1

2.4) Equations

Current State Bits: Q2, Q1, Q0

Next State Bits: D2, D1, D0

Input Bits: Pq, Ph, Pdr, Pdw

2.4.1) Next State Equations

$$D2 = Q2' \cdot Q1' \cdot Q0' \cdot Pq' \cdot Ph' \cdot Pdr' \cdot Pdw$$

$$D1 = (Q2' \cdot Q1' \cdot Q0' \cdot Pq' \cdot Ph) + (Q2' \cdot Q1' \cdot Q0' \cdot Pq' \cdot Ph' \cdot Pdr)$$

$$D0 = (Q2' \cdot Q1' \cdot Q0' \cdot Pq) + (Q2' \cdot Q1' \cdot Q0' \cdot Pq' \cdot Ph' \cdot Pdr)$$

2.4.2) Output Equations

$$\text{QuickWash_Request} = Q2' \cdot Q1' \cdot Q0$$

$$\text{HeavyWash_Request} = Q2' \cdot Q1 \cdot Q0'$$

$$\text{Dryer_Request} = Q2' \cdot Q1 \cdot Q0$$

$$\text{DelicateWash_Request} = Q2 \cdot Q1' \cdot Q0'$$

2.5) FSM State Transition Diagram

 


Figure 1. FSM Diagram

Starting from **S0_IDLE**, the FSM processes requests sequentially using fixed priority (Quick > Heavy > Dryer > Delicate). It enters a request state for exactly one cycle to trigger the datapath and then returns to IDLE. This pulse-based logic, combined with edge detection, ensures each button press is handled exactly once, maintaining system stability.

2.6) FSM Schematic

 


Figure 2. FSM Schematic

2.7) Datapath Schematic

The datapath consists of four parallel units managing machine status, waiting queues, and specific service durations (4s, 7s, 9s, 11s). When a request signal arrives, the machine starts immediately if idle; otherwise, the request increments the queue counter. Integrated feedback loops ensure that the next waiting request starts automatically once a machine completes its cycle, ensuring continuous operation.

 


Figure 3. Datapath

Question 3) Determine the minimum number of flip-flops required by your encoding.

The minimum number of flip-flops required for the FSM state encoding is **3**.

Explanation: Our FSM design consists of 5 distinct states. Since 2 flip-flops can only represent $2^2 = 4$ states, they are insufficient. Using 3 flip-flops provides $2^3 = 8$ possible combinations, which is the minimum number required to successfully encode our 5 states.

It is important to note that these 3 flip-flops are only for the FSM. A significant number of additional flip-flops are required for the datapath. Specifically, the datapath contains 4 separate single-bit flip-flops to track the busy status of each machine, as well as many more internal flip-flops located within the Queue Counters and Timers.

Question 4) Redesign your outputs using decoders to simplify the combinational logic. Use a 3-to-8 decoder to generate one-hot encoded state signals from your state register bits, then express your output functions in terms of these decoded signals.

 


Figure 4. FSM design with decoder

Decoder Output Table

State Name	Encoding (Q2Q1Q0)	Decoder Output (Yn)

SO_IDLE	000	Y0
S_REQ_QUICKWASH	001	Y1
S_REQ_HEAVYWASH	010	Y2
S_REQ_DRYER	011	Y3
S_REQ_DELICATEWASH	100	Y4

QuickWash_Request = Y1

HeavyWash_Request = Y2

Dryer_Request = Y3

DelicateWash_Request = Y4

By using a 3-to-8 decoder, we convert the binary state bits into one-hot encoded signals. This eliminates the need for complex logic gates (AND/OR/NOT) to generate the outputs, as each service request signal can now be directly connected to its corresponding decoder output pin.

 


Figure 5. Top-Level RTL Schematic of the Smart Laundry Controller

 


Figure 6. Detailed RTL Schematic of the Smart Laundry Controller

 


Figure 7. Clock Divider

Question 5) Write a SystemVerilog module implementing your FSM and a self-checking testbench that verifies functionality.

SystemVerilog Module

```
`timescale 1ns / 1ps
```

```
// Signal Stabilizer Core
```

```
module Signal_Stabilizer_Core (
```

```
    input logic clk_sys_mhz,
```

```
    input logic raw_btn_in,
```

```
    output logic clean_pulse_out
```

```
);
```

```
    logic [19:0] stabilization_cnt;
```

```
    logic current_st;
```

```
    logic previous_st;
```

```
always_ff @(posedge clk_sys_mhz) begin
```

```
    previous_st <= current_st;
```

```
    if (raw_btn_in == current_st) begin
```

```
        stabilization_cnt <= 0;
```

```
    end else begin
```

```
        stabilization_cnt <= stabilization_cnt + 1;
```

```
        if (stabilization_cnt == 20'd1_000_000) begin
```

```
            current_st <= raw_btn_in;
```

```
            stabilization_cnt <= 0;
```

```
        end
```

```
    end
```

```
end
```

```

    assign clean_pulse_out = (current_st == 1'b1) && (previous_st == 1'b0);
endmodule

```

```
// Button Signal Conditioner
```

```

module Button_Signal_Conditioner (
    input logic clk_sys_mhz,
    input logic buttonFirst, buttonSecond, buttonThird, buttonFourth,
    output logic pls_qw, pls_hw, pls_dr, pls_dw
);
    Signal_Stabilizer_Core filter_qw (.clk_sys_mhz(clk_sys_mhz),
    .raw_btn_in(buttonFirst), .clean_pulse_out(pls_qw));
    Signal_Stabilizer_Core filter_hw (.clk_sys_mhz(clk_sys_mhz),
    .raw_btn_in(buttonSecond), .clean_pulse_out(pls_hw));
    Signal_Stabilizer_Core filter_dr (.clk_sys_mhz(clk_sys_mhz),
    .raw_btn_in(buttonThird), .clean_pulse_out(pls_dr));
    Signal_Stabilizer_Core filter_dw (.clk_sys_mhz(clk_sys_mhz),
    .raw_btn_in(buttonFourth), .clean_pulse_out(pls_dw));
endmodule

```

```
// Clock Freq Divider
```

```

module Clk_Freq_Divider (
    input logic clk_sys_mhz, rstt_sys_n,
    output logic blink_led_sig
);
    logic [25:0] tick_counter;
    always_ff @(posedge clk_sys_mhz or posedge rstt_sys_n) begin
        if (rstt_sys_n) begin
            tick_counter <= 0;

```

```

        blink_led_sig <= 0;
    end else begin
        if (tick_counter == 25_000_000 - 1) begin
            tick_counter <= 0;
            blink_led_sig <= ~blink_led_sig;
        end else begin
            tick_counter <= tick_counter + 1;
        end
    end
end
endmodule

```

// State Decoder

```

module State_Decoder_3to8 (
    input logic [2:0] state_in_bits,
    output logic [7:0] decoded_out_onehot
);
    always_comb begin
        decoded_out_onehot = 8'b00000000;
        decoded_out_onehot[state_in_bits] = 1'b1;
    end
endmodule

```

// FSM LndryMachine

```

module FSM_LndryMachine (
    input logic clk_sys_mhz, rstt_sys_n,

```

```

input logic pls_qw, pls_hw, pls_dr, pls_dw,
output logic req_quick_w, req_heavy_w, req_dryer_m, req_delicate_w
);

typedef enum logic [2:0] {
    IDLE_ST = 3'b000, REQ_Q_ST = 3'b001, REQ_H_ST = 3'b010,
    REQ_DR_ST = 3'b011, REQ_DW_ST = 3'b100
} sys_state_t;

sys_state_t st_current, st_next;

always_ff @(posedge clk_sys_mhz or posedge rstt_sys_n) begin
    if (rstt_sys_n) st_current <= IDLE_ST;
    else st_current <= st_next;
end

always_comb begin
    st_next = IDLE_ST;
    case (st_current)
        IDLE_ST: begin
            if (pls_qw)    st_next = REQ_Q_ST;
            else if (pls_hw) st_next = REQ_H_ST;
            else if (pls_dr) st_next = REQ_DR_ST;
            else if (pls_dw) st_next = REQ_DW_ST;
        end
        default: st_next = IDLE_ST;
    endcase

```

end

// Decoder Usage

logic [7:0] decoder_wire;

State_Decoder_3to8 dec_inst (

 .state_in_bits(st_current),

 .decoded_out_onehot(decoder_wire)

);

assign req_quick_w = decoder_wire[1];

assign req_heavy_w = decoder_wire[2];

assign req_dryer_m = decoder_wire[3];

assign req_delicate_w = decoder_wire[4];

endmodule

// Laundry Execution Datapath

module Laundry_Execution_Datapath #(parameter integer PROC_DUR = 4) (

 input logic clk_sys_mhz, rstt_sys_n, req_in_sig,

 output logic is_busy_flag

);

logic [2:0] wait_queue;

logic [3:0] sec_timer;

logic [26:0] sec_scaler;

logic tick_1s;

assign tick_1s = (sec_scaler == 100_000_000 - 1);

```
always_ff @(posedge clk_sys_mhz or posedge rstt_sys_n) begin
    if (rstt_sys_n) begin
        is_busy_flag <= 0; wait_queue <= 0; sec_timer <= 0; sec_scaler <= 0;
    end else begin

        if (is_busy_flag) begin
            if (tick_1s) sec_scaler <= 0;
            else sec_scaler <= sec_scaler + 1;
        end else begin
            sec_scaler <= 0;
        end

        if (!is_busy_flag) begin
            if (req_in_sig) begin
                is_busy_flag <= 1;
                sec_timer <= PROC_DUR;
            end else if (wait_queue > 0) begin
                is_busy_flag <= 1;
                sec_timer <= PROC_DUR;
                wait_queue <= wait_queue - 1;
            end

            end else begin
                if (req_in_sig && wait_queue < 7) begin
                    wait_queue <= wait_queue + 1;
                end
            end
        end
    end
```



```

        if (tick_1s) begin
            if (sec_timer > 1) begin
                sec_timer <= sec_timer - 1;
            end else begin
                is_busy_flag <= 0;
            end
        end
    end
end

end
end
endmodule

// Busy State Aggregator
module Busy_State_Aggregator (
    input logic st_qw, st_hw, st_dr, st_dw,
    output logic [2:0] total_active_cnt
);
    assign total_active_cnt = st_qw + st_hw + st_dr + st_dw;
endmodule

// Main System Wrapper
module laundry_top (
    input logic clk_sys_mhz, rstt_sys_n,
    input logic buttonFirst, buttonSecond, buttonThird, buttonFourth,

```

```

output logic [15:0] led,
output logic [6:0] seg,
output logic dp,
output logic [3:0] an
);

logic pls_qw, pls_hw, pls_dr, pls_dw;
logic req_quick_w, req_heavy_w, req_dryer_m, req_delicate_w;
logic blink_led_sig;
logic flag_qw, flag_hw, flag_dr, flag_dw;
logic [2:0] sum_active_mach;

// Filter Group
Button_Signal_Conditioner btn_filter_blk (
    .clk_sys_mhz(clk_sys_mhz),
    .buttonFirst(buttonFirst), .buttonSecond(buttonSecond),
    .buttonThird(buttonThird), .buttonFourth(buttonFourth),
    .pls_qw(pls_qw), .pls_hw(pls_hw), .pls_dr(pls_dr), .pls_dw(pls_dw)
);

// Clock Mod
Clk_Freq_Divider clk_mod_blk (
    .clk_sys_mhz(clk_sys_mhz), .rstt_sys_n(rstt_sys_n),
    .blink_led_sig(blink_led_sig)
);

// FSM Controller
FSM_LndryMachine fsm_ctrl_blk (

```

```

        .clk_sys_mhz(clk_sys_mhz), .rstt_sys_n(rstt_sys_n),
        .pls_qw(pls_qw), .pls_hw(pls_hw), .pls_dr(pls_dr), .pls_dw(pls_dw),
        .req_quick_w(req_quick_w), .req_heavy_w(req_heavy_w),
        .req_dryer_m(req_dryer_m), .req_delicate_w(req_delicate_w)
    );

```

```
// QuickWashMachine Datapath
```

```

    Laundry_Execution_Datapath #(4) QuickWashMachine_Datapath (
        .clk_sys_mhz(clk_sys_mhz), .rstt_sys_n(rstt_sys_n),
        .req_in_sig(req_quick_w), .is_busy_flag(flag_qw)
    );

```

```
// HeavyWashMachine Datapath
```

```

    Laundry_Execution_Datapath #(7) HeavyWashMachine_Datapath (
        .clk_sys_mhz(clk_sys_mhz), .rstt_sys_n(rstt_sys_n),
        .req_in_sig(req_heavy_w), .is_busy_flag(flag_hw)
    );

```

```
// DryerMachine Datapath
```

```

    Laundry_Execution_Datapath #(9) DryerMachine_Datapath (
        .clk_sys_mhz(clk_sys_mhz), .rstt_sys_n(rstt_sys_n),
        .req_in_sig(req_dryer_m), .is_busy_flag(flag_dr)
    );

```

```
// DelicateWashMachine Datapath
```

```

    Laundry_Execution_Datapath #(11) DelicateWashMachine_Datapath (
        .clk_sys_mhz(clk_sys_mhz), .rstt_sys_n(rstt_sys_n),
        .req_in_sig(req_delicate_w), .is_busy_flag(flag_dw)
    );

```

```
);
```

```
// RTL Adder Equivalent
```

```
Busy_State_Aggregator sum_calc_blk (
```

```
    .st_qw(flag_qw), .st_hw(flag_hw), .st_dr(flag_dr), .st_dw(flag_dw),
```

```
    .total_active_cnt(sum_active_mach)
```

```
);
```

```
// LED Outputs
```

```
assign led[14:12] = flag_qw ? {3{blink_led_sig}} : 3'b111;
```

```
assign led[10:8] = flag_hw ? {3{blink_led_sig}} : 3'b111;
```

```
assign led[6:4] = flag_dr ? {3{blink_led_sig}} : 3'b111;
```

```
assign led[2:0] = flag_dw ? {3{blink_led_sig}} : 3'b111;
```

```
assign led[15] = 0; assign led[11] = 0; assign led[7] = 0; assign led[3] = 0;
```

```
// Seven Segment
```

```
assign an = 4'b1110;
```

```
assign dp = 1;
```

```
always_comb begin
```

```
    case (sum_active_mach)
```

```
        3'd0: seg = 7'b1000000;
```

```
        3'd1: seg = 7'b1111001;
```

```
        3'd2: seg = 7'b0100100;
```

```
        3'd3: seg = 7'b0110000;
```

```
        3'd4: seg = 7'b0011001;
```

```

        default: seg = 7'b1111111;
    endcase
end
endmodule

```

Testbench 1

```
`timescale 1ns / 1ps
```

```
module tb_FSM_LndryMachine();
```

```
    logic clk_sys_mhz;
```

```
    logic rstt_sys_n;
```

```
    logic pls_qw, pls_hw, pls_dr, pls_dw;
```

```
    logic req_quick_w, req_heavy_w, req_dryer_m, req_delicate_w;
```

```
    FSM_LndryMachine uut (
```

```
        .clk_sys_mhz(clk_sys_mhz),
```

```
        .rstt_sys_n(rstt_sys_n),
```

```
        .pls_qw(pls_qw), .pls_hw(pls_hw), .pls_dr(pls_dr), .pls_dw(pls_dw),
```

```
        .req_quick_w(req_quick_w), .req_heavy_w(req_heavy_w),
```

```
        .req_dryer_m(req_dryer_m), .req_delicate_w(req_delicate_w)
```

```
    );
```

```
always #5 clk_sys_mhz = ~clk_sys_mhz;
```

```
initial begin
```

```
    clk_sys_mhz = 0;
```

```
    rstt_sys_n = 1;
```

```
    pls_qw = 0; pls_hw = 0; pls_dr = 0; pls_dw = 0;
```

```
    #50;
```

```
    rstt_sys_n = 0;
```

```
    #50;
```

```
    @(posedge clk_sys_mhz);
```

```
    pls_qw = 1;
```

```
    @(posedge clk_sys_mhz);
```

```
    pls_qw = 0;
```

```
    #100;
```

```
@(posedge clk_sys_mhz);  
pls_hw = 1;  
  
@(posedge clk_sys_mhz);  
pls_hw = 0;
```

```
#100;
```

```
@(posedge clk_sys_mhz);  
pls_dr = 1; pls_dw = 1;  
  
@(posedge clk_sys_mhz);  
pls_dr = 0; pls_dw = 0;
```

```
#100;
```

```
#200;
```

```
$finish;
```

```
end
```

```
endmodule
```

Testbench 2

```
`timescale 1ns / 1ps
```

```
module tb_FSM_LndryMachine();
```

```
    logic clk_sys_mhz;
```

```
    logic rstt_sys_n;
```

```
    logic pls_qw, pls_hw, pls_dr, pls_dw;
```

```
    logic req_quick_w, req_heavy_w, req_dryer_m, req_delicate_w;
```

```
    FSM_LndryMachine uut (
```

```
        .clk_sys_mhz(clk_sys_mhz),
```

```
        .rstt_sys_n(rstt_sys_n),
```

```
        .pls_qw(pls_qw), .pls_hw(pls_hw), .pls_dr(pls_dr), .pls_dw(pls_dw),
```

```
        .req_quick_w(req_quick_w), .req_heavy_w(req_heavy_w),
```

```
        .req_dryer_m(req_dryer_m), .req_delicate_w(req_delicate_w)
```

```
    );
```

```
    always #5 clk_sys_mhz = ~clk_sys_mhz;
```

```
    initial begin
```

```
        clk_sys_mhz = 0;
```

```
        rstt_sys_n = 1;
```

```
        pls_qw = 0; pls_hw = 0; pls_dr = 0; pls_dw = 0;
```

```
        #20 rstt_sys_n = 0;
```



```
$display("FSM TEST STARTED");
```

```
@(posedge clk_sys_mhz);
```

```
pls_qw = 1;
```

```
@(posedge clk_sys_mhz);
```

```
pls_qw = 0;
```

```
#1;
```

```
if (req_quick_w === 1'b1)
```

```
    $display("Quick Wash request handled correctly.");
```

```
else
```

```
    $display("Quick Wash request failed!");
```

```
@(posedge clk_sys_mhz);
```

```
#1;
```

```
if (req_quick_w === 1'b0)
```

```
    $display("Returned to IDLE state.");
```

```
else
```

```
    $display("FSM failed to return to IDLE!");
```

```
#50;
```

```
@(posedge clk_sys_mhz);
```

```
pls_hw = 1; pls_dr = 1;
```

```
@(posedge clk_sys_mhz);
```

```
pls_hw = 0; pls_dr = 0;
```

```

#1;
if (req_heavy_w === 1'b1 && req_dryer_m === 1'b0)
    $display("Priority rule passed.");
else
    $display("Priority rule violated!");

#50;

@(posedge clk_sys_mhz);
pls_qw = 1; pls_hw = 1; pls_dr = 1; pls_dw = 1;
@(posedge clk_sys_mhz);
pls_qw = 0; pls_hw = 0; pls_dr = 0; pls_dw = 0;

#1;
if (req_quick_w === 1'b1 && req_delicate_w === 1'b0)
    $display("Full load priority passed.");
else
    $display("Full load priority failed!");

#50;
$display("ALL TESTS COMPLETED.");
$finish;
end

endmodule

```

